

# THE UNIVERSITY OF TEXAS AT DALLAS



## Electromagnetic Engineering I

### EE 4301

### Spring 2008 Assignment 10

#### Due Date and Time:

At 9:30 AM, March 31, 2008

#### Reading:

N. N. Rao, *Elements of Engineering Electromagnetics*, **Sixth Edition**, Chapter 6

#### Problems:

Please write your answers to the following problems on engineering paper. No credit will be given for work handed in on other types of paper.

1. A parallel-plate transmission line has the following parameters: Material of plates is aluminum (conductivity  $\sigma = 3.54 \times 10^7 \text{ S/m}$ ), plate thickness is  $h = 0.1 \text{ } \mu\text{m}$ , length  $l = 100 \text{ } \mu\text{m}$ , width  $w = 1.0 \text{ } \mu\text{m}$ , plate separation  $d = 0.1 \text{ } \mu\text{m}$ , permittivity of the dielectric between the plates  $\epsilon = 4.0 \epsilon_0$ , permeability of the dielectric between the plates  $\mu = \mu_0$ .
  - (a) Find the inductance per unit length,  $L'$ .
  - (b) Find the capacitance per unit length,  $C'$ .
  - (c) Find the characteristic impedance,  $Z_0$ .
  - (d) Find the one-way transit time for this transmission line.
2. Design a parallel-plate transmission line such that  $\epsilon_r = 4$ ,  $\mu_r = 1$ ,  $w = 0.5 \text{ mm}$ , and  $Z_0 = 75 \text{ } \Omega$ . (Your design must specify the spacing,  $d$ .)
3. You are given the information that a certain transmission line has a characteristic impedance of  $225 \text{ } \Omega$ , and that the load is an antenna. What is the reflection coefficient at the load if the antenna's impedance is  $75 \text{ } \Omega$ ?

Exercises 4–8 concern a transmission line with the following parameters: Source impedance =  $100\ \Omega$ , load impedance =  $25\ \Omega$ , characteristic impedance =  $50\ \Omega$ , velocity of electromagnetic waves =  $2 \times 10^8\ \text{m/s}$ , length =  $6\ \text{m}$ .

4. What is the transit time  $T$  from one end of the line to the other?
5. Draw a bounce diagram from time  $t = 0$  to time  $t = 3T$  showing  $V_+$  and  $V_-$  as functions of  $z$  and  $t$ , assuming that a short pulse with amplitude  $5\ \text{V}$ , traveling towards  $+Z$ , is injected instantaneously at  $z = 0$  and at time  $t = 0$ .
6. Repeat Problem 5 when the source is a 5-volt battery that is connected to the source end of the transmission line at  $t = 0$  and is left connected indefinitely.
7. Plot the total voltage at the load end ( $z = 6\ \text{m}$ ) as a function of time from  $t = 0$  to  $t = 3T$ .
8. Plot the total voltage at  $z = 4\ \text{m}$  as a function of time from  $t = 0$  to  $t = 3T$ .
9. Consider an ideal parallel-plate transmission line with the following parameters: Length =  $9\ \text{cm}$ , relative permittivity of the dielectric medium between the plates =  $4$ , characteristic impedance =  $30\ \Omega$ , internal impedance of source =  $20\ \Omega$ , load impedance =  $60\ \Omega$ , source voltage =  $5\ \text{V}$ . Find the velocity of electromagnetic waves on the transmission line, and the one-way transit time,  $T$ .
10. For the transmission line in Problem 9, find the reflection coefficients at the source and load ends.
11. For the transmission line in Problem 9, draw a bounce diagram from time  $t = 0$  to time  $t = 3T$  showing  $V_+$  and  $V_-$  as functions of  $z$  and  $t$ , assuming that a source voltage of  $5\ \text{V}$  is turned on instantaneously at time  $t = 0$ .
12. For the transmission line in Problem 9, plot the total voltage at the load end ( $z = 9\ \text{cm}$ ) as a function of time from  $t = 0$  to  $t = 3T$ .

13. A transmission line formed by an aluminum trace, an  $\text{SiO}_2$  insulating layer and a Si substrate has the following parameters:

$$\text{Length } l = 10^{-3}\ \text{m} = 1000\ \mu\text{m}$$

$$\text{Phase velocity } v = 2 \times 10^8\ \text{m/s} = 200\ \mu\text{m/ps}$$

$$\text{Characteristic impedance } Z_0 = 50\ \Omega$$

This transmission line is unterminated at the load end, and is driven by a very-low-impedance source. The resulting reflection coefficients are

$$\rho_S = -0.8, \quad \rho_L = 1.0.$$

The signal risetime is  $T_{\text{rise}} = 20\ \text{ps}$ .

- (a) Would you expect to see significant overshoot or ringing after a time duration of two risetimes, given this signal and transmission line? [Hint: Compare the round-trip transit time,

$$2T = 2\frac{l}{v},$$

with twice the signal risetime,  $2T_{\text{rise}}$ .]

- (b) According to the criterion<sup>1</sup> that a transmission line is *not* short if

$$l > \frac{1}{6}vT_{\text{rise}},$$

is the transmission line described in this problem short? Justify your answer.

- (c) Using the formula<sup>2</sup>

$$t_{\text{settle}} \approx 2T \frac{\ln \epsilon}{\ln |\rho_S \rho_L|}$$

for the time for the signal to settle to within a fraction  $\epsilon < 1$  of its final value, evaluate the settling time  $t_{\text{settle}}$  for the transmission line and signal considered in this problem. Is  $t_{\text{settle}}$  greater, or less, than the signal risetime  $T_{\text{rise}}$ ?

<sup>1</sup>Howard W. Johnson and Martin Graham, *High-Speed Digital Design* (Prentice-Hall, 1993), p. 166

<sup>2</sup>Howard W. Johnson and Martin Graham, *High-Speed Digital Design* (Prentice-Hall, 1993), p. 167