

Worksheet # 2A: DeMorgan's Law and Using K-Maps for Simplification

DeMorgan's Law states the following two equivalences:

1. $\overline{x + y} = \overline{x} \cdot \overline{y}$, (OR version of DeMorgan's Law), and
2. $\overline{x \cdot y} = \overline{x} + \overline{y}$ (AND version of DeMorgan's Law).

Let us consider these separately. We can also express $\overline{x \cdot y} = \overline{x} + \overline{y}$ as $\overline{\overline{x \cdot y}} = \overline{\overline{x} + \overline{y}}$ (taking the complement of both sides, so that this does not change the relation). Thus, since we know that $\overline{\overline{x}} = x$, then we can say that the AND version of DeMorgan's law can also be expressed as:

$$3. \underline{\underline{x \cdot y = \overline{\overline{x} + \overline{y}}}}$$

And likewise, the OR version, $\overline{x + y} = \overline{x} \cdot \overline{y}$ can be expressed as:

$$4. \underline{\underline{x + y = \overline{\overline{x} \cdot \overline{y}}}}$$

Incidentally, these two expressions are the proof that NAND and AND-NOT are not the same functions, and that NOR and OR-NOT are also not the same functions. Now, using the different forms of DeMorgan's Law above, find simpler versions of the following Boolean expressions:

- $f = x \cdot \left[\overline{\overline{y + x}} \right]$

- $f = x + \left[\overline{\overline{y \cdot x}} \right]$

- $f = \overline{x \cdot y} + \overline{w \cdot z}$

Simplification Using Karnaugh-Maps:

- Given the Boolean function $f = xy\bar{z} + x\bar{y}z + xyz$, plot the 1's on the K-Map below, find the simplified SOP function, and plot the simplified SOP circuit.

		yz			
		00	01	11	10
x	0				
	1				

- Given the truth table, use the K-Map to develop a simplified POS expression and draw the simplified POS circuit.

		y + z			
		00	01	11	10
w + x	00				
	01				
	11				
	10				

w	x	y	z	f
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	
0	1	1	0	
0	1	1	1	
1	0	0	0	0
1	0	0	1	
1	0	1	0	
1	0	1	1	
1	1	0	0	0
1	1	0	1	
1	1	1	0	
1	1	1	1	

- A Boolean function is defined on a 4-D K-Map as $f = \sum_m 0,2,4,6$. Plot the 1's on the K-Map below, simplify in SOP form as much as possible, and draw the simplified SOP circuit.

		yz			
		00	01	11	10
wx	00				
	01				
	11				
	10				