

EE7326.501
Homework # 2

Due: Monday, September 29

Do problem 10.8, page 444 in your textbook. Find the Z domain transfer function, $H(Z)$, assuming the opamp has a infinite voltage gain. Be sure to use the component labels in Fig. P10.8 so that your derivation can be followed.